



电路

任课教师：魏佩瑜教授
电工电子教研室

1.

5

(

)

98

07

0712

071201

071202

*071203**

08

0806

080601

080602

080603

080604

080605

080606

080607

(

(

)

)



}

(

)

2.

3.



4


4

8

14

15

3

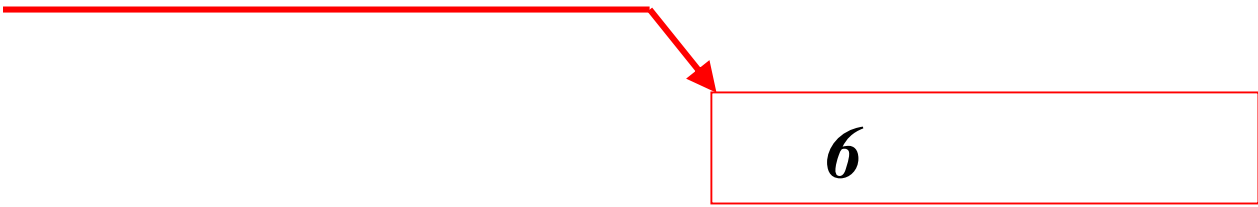


6









1.

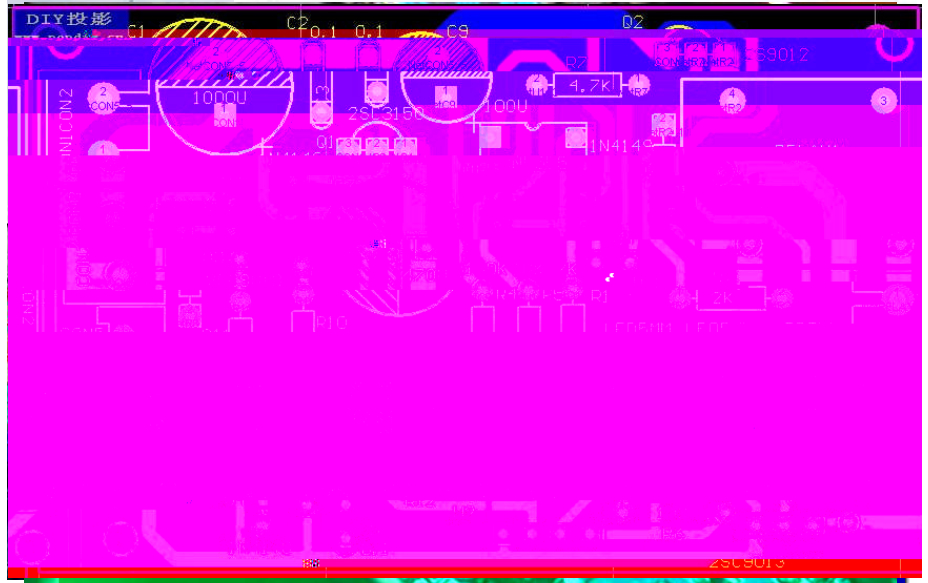


2.

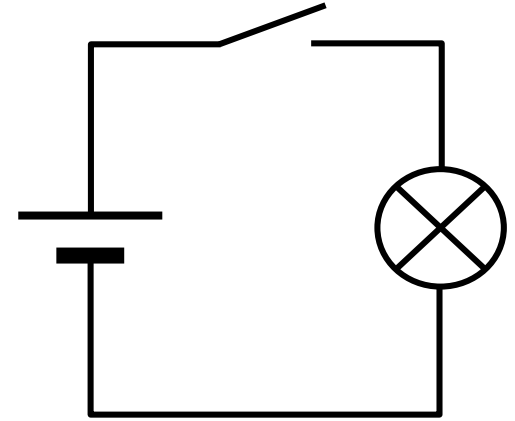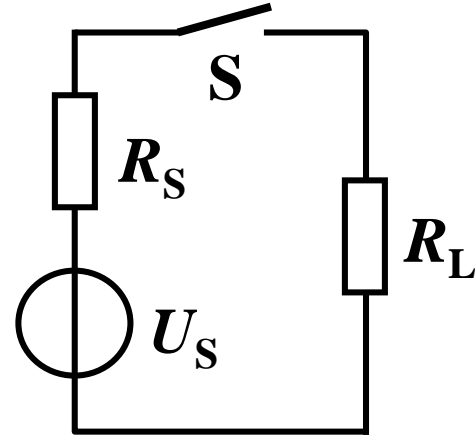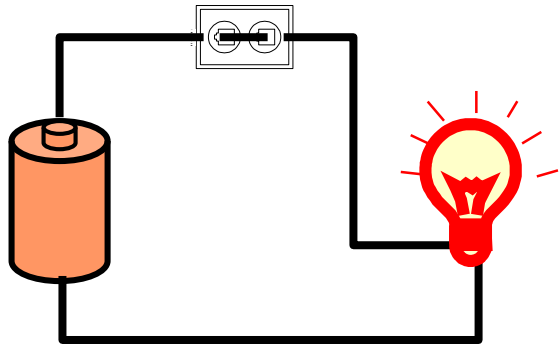


()

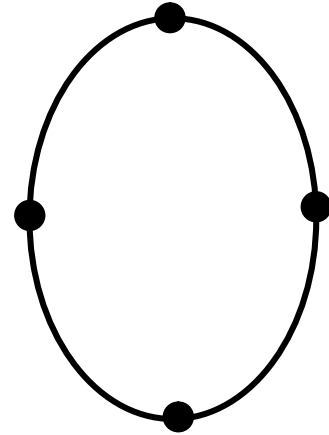

 **5**



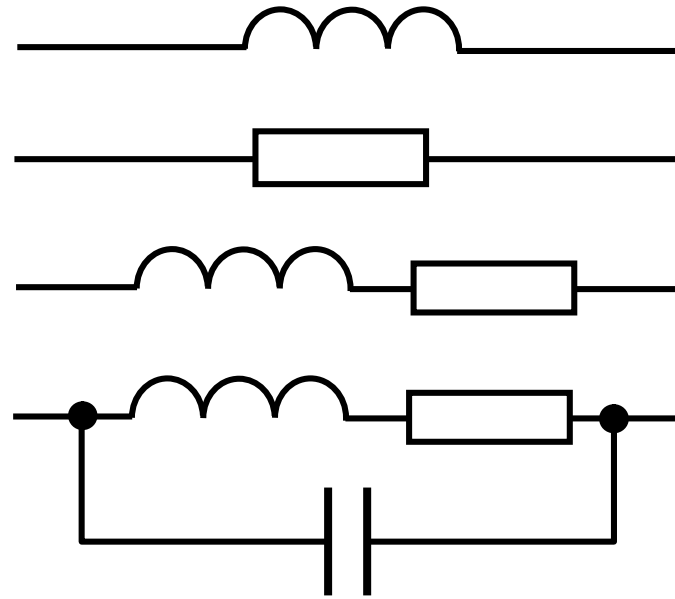

1 2



-
-





$$i(t) = \frac{dq(t)}{dt} = \lim_{\Delta t \rightarrow 0} \frac{q(t) - q(t - \Delta t)}{\Delta t}$$




- **A () kA mA A**

$$1 \text{ kA} = 10^3 \text{ A} \quad 1 \text{ mA} = 10^{-3} \text{ A} \quad 1 \text{ A} = 10^0 \text{ A}$$

•

()

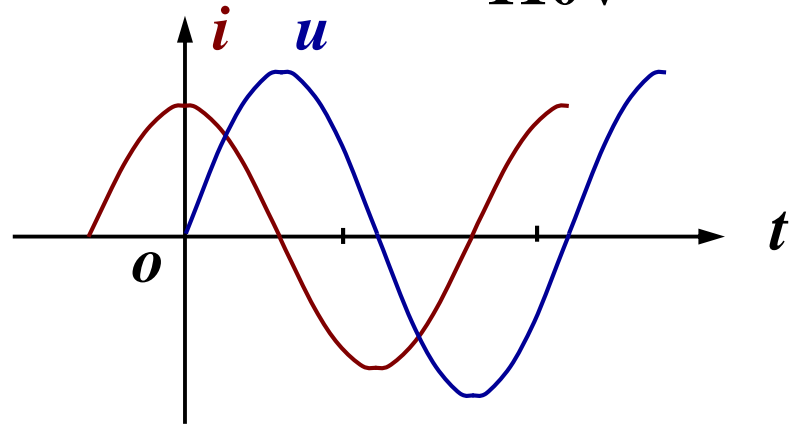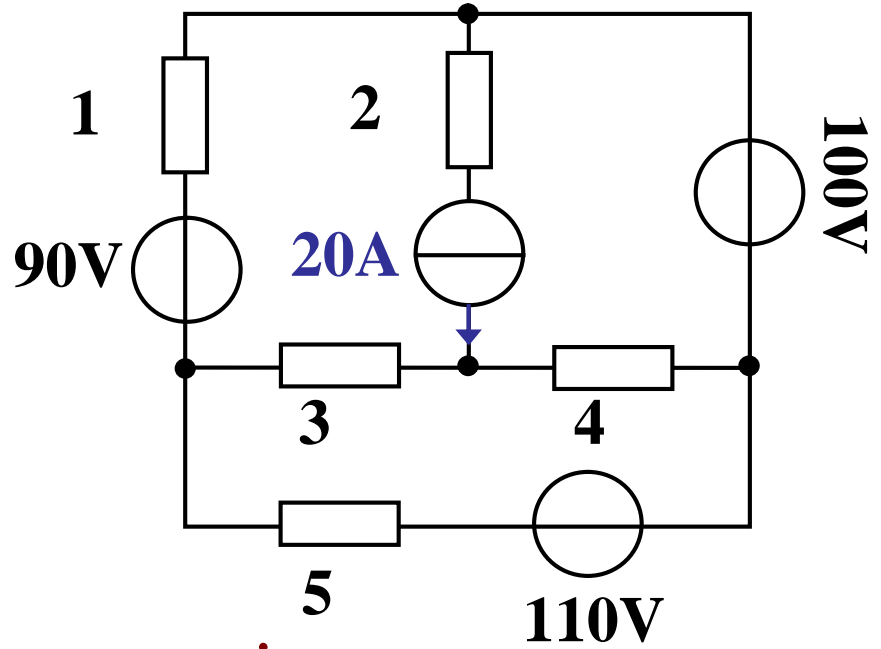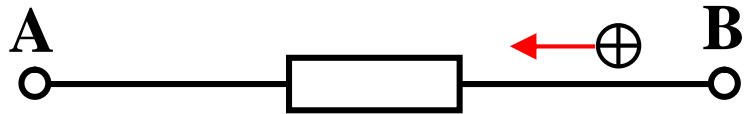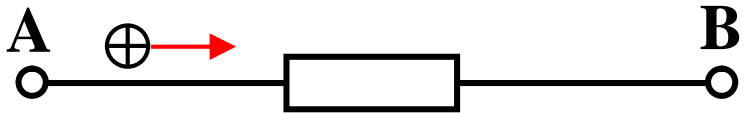

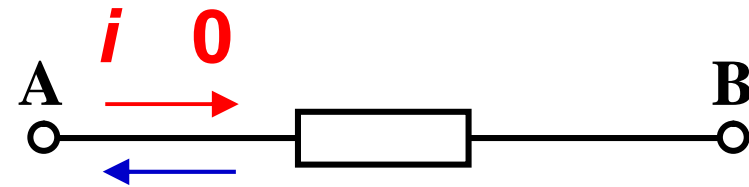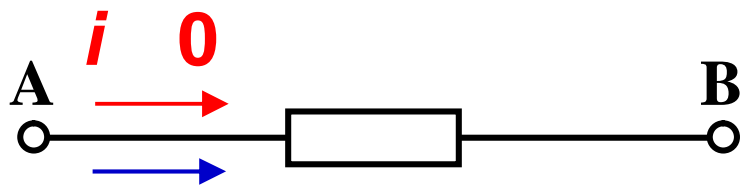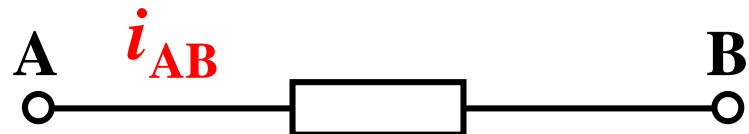

()

()

A

B

i_{AB}

2.


- q
 - $(=0)$
 - U
- (W)

$$U = \frac{dW}{dq}$$


- V () kV mV V

(1) $4C$ $8J$ $12J$
 U_{ab} U_{bc}

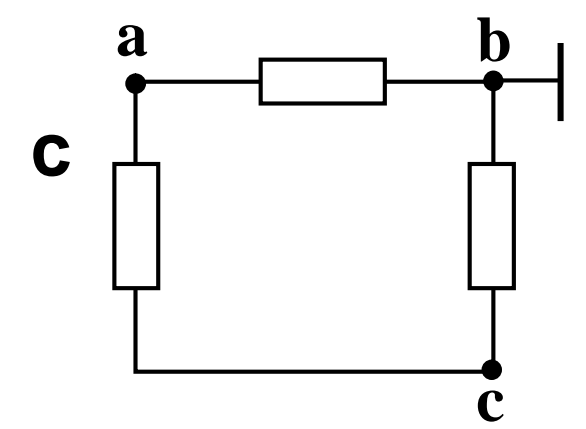(2) 0
 $\frac{W_{ac}}{q} = \frac{(8 + 12)}{4} = 5V$
 $\frac{W_{bc}}{q} = \frac{12}{4} = 3V$




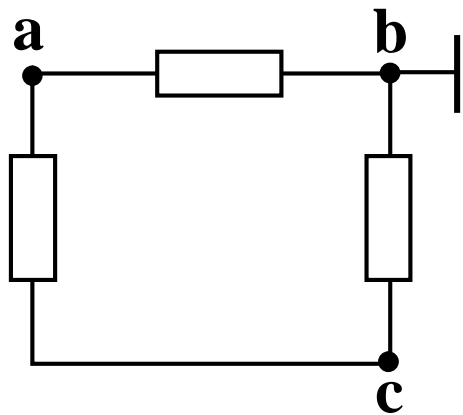$U_{ab} = 5 - 3 = 2V$
 $U_{bc} = 3 - 3 = 0V$



b **0** a **2V** c **3V**

U_{ab} **2V** U_{bc} **3V**

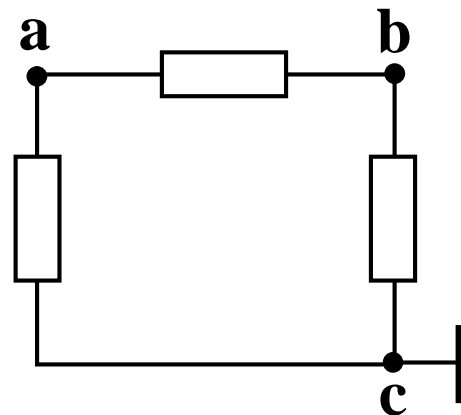

c **0** a **5V** b **3V**

U_{ab} **2V** U_{bc} **3V**






-

()

()



(1)

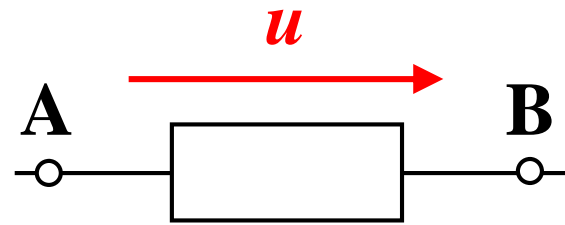

(2)





(3)



3.




u i

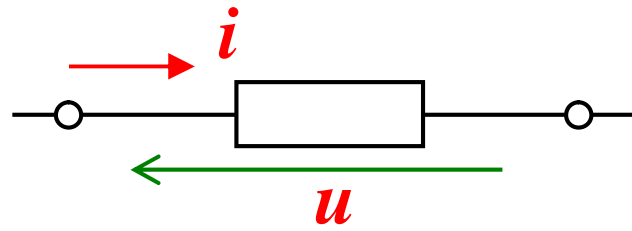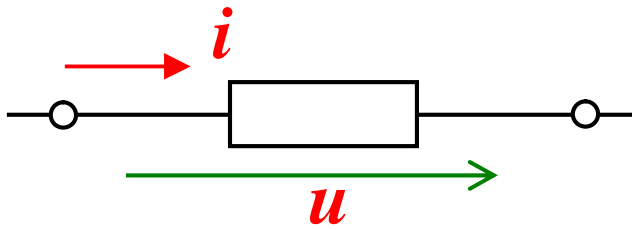

A **B**

A

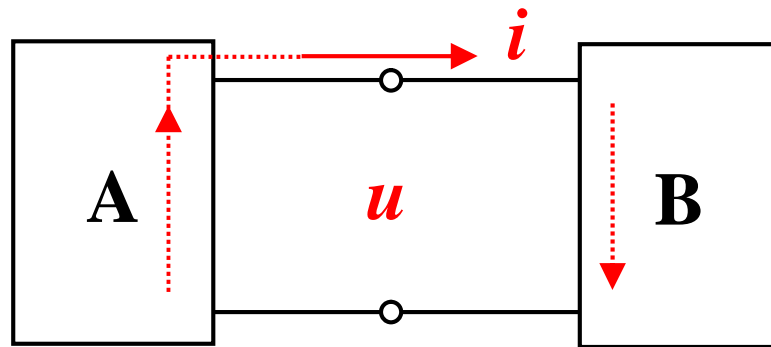

B



1 3



1.


$$p \frac{dw}{dt} \quad u \frac{dw}{dq} \quad i \frac{dq}{dt}$$

$$p \frac{dw}{dt} \quad \frac{dw}{dq} \frac{dq}{dt} \quad ui \quad p \quad ui$$


W () (Watt) kW mW

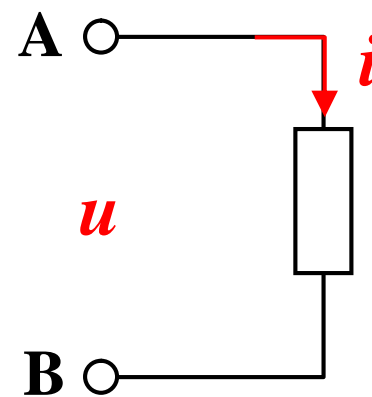2.


$$\begin{array}{l} \text{Ⓢ} \quad u \quad i \\ p \quad ui \\ p \quad 0 \\ p \quad 0 \end{array} \quad \begin{array}{l} (\quad) \\ (\quad) \end{array}$$


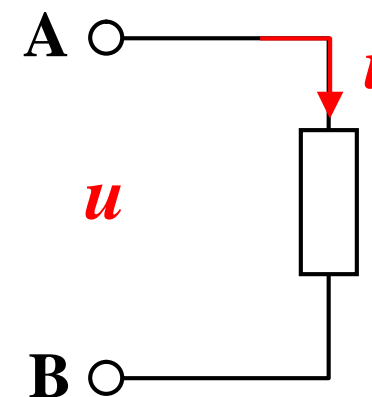
$$\begin{array}{l} \text{Ⓢ} \quad u \quad i \\ p \quad ui \\ p \quad 0 \\ p \quad 0 \end{array} \quad \begin{array}{l} (\quad) \\ (\quad) \end{array}$$



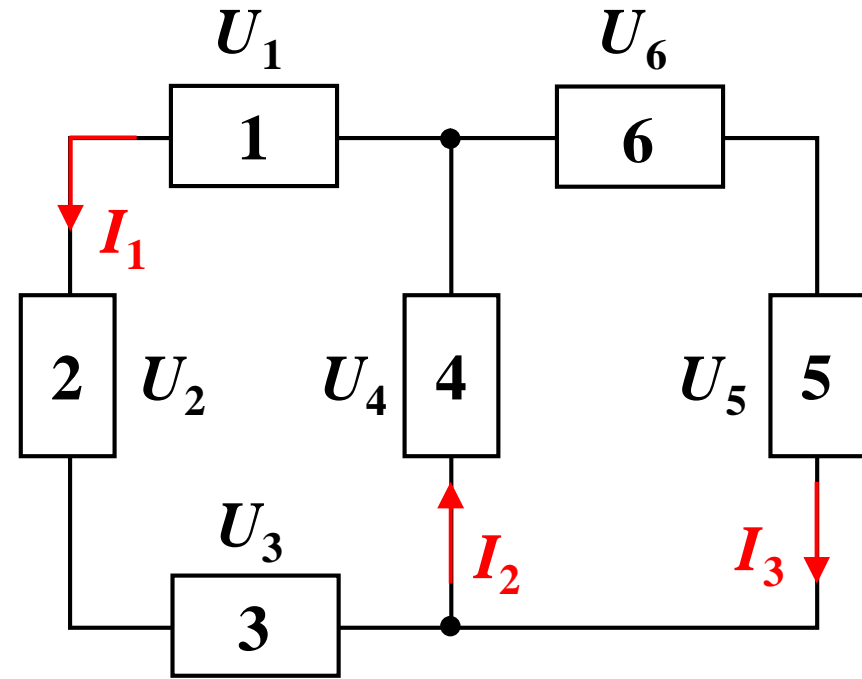U_1 1V U_2 3V
 U_3 8V U_4 4V
 U_5 7V U_6 3V
 I_1 2A I_2 1A I_3 1A



P_1 $U_1 I_1$ 1 2 2W

P_2 $U_2 I_1$ 2 6W

P_3 $U_3 I_1$ 2 6W

P_4 $U_4 I_2$ 4W

P_5 $U_5 I_3$ 7W

P_6 $U_6 I_3$ 3W



3.

$$p = \frac{dw}{dt}$$

$$dw = p dt = u i dt$$

t_0 t

$$w(t) = \int_{t_0}^t u(\tau) i(\tau) d\tau$$

J () (**Joule**)

1 4

1.



5





5

“

”

()

()

2.



$$d \ll$$



$$f = 20\text{kHz}$$

$$v = 3 \cdot 10^8 \text{ m/s}$$

$$\frac{v}{f} = 15\text{km}$$



“ ”

“ ”


(

)

(18)



u i

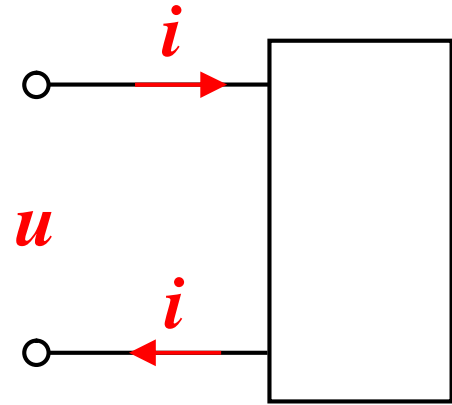


1 5

1.


u i

$f(u,i)$ 0 ←

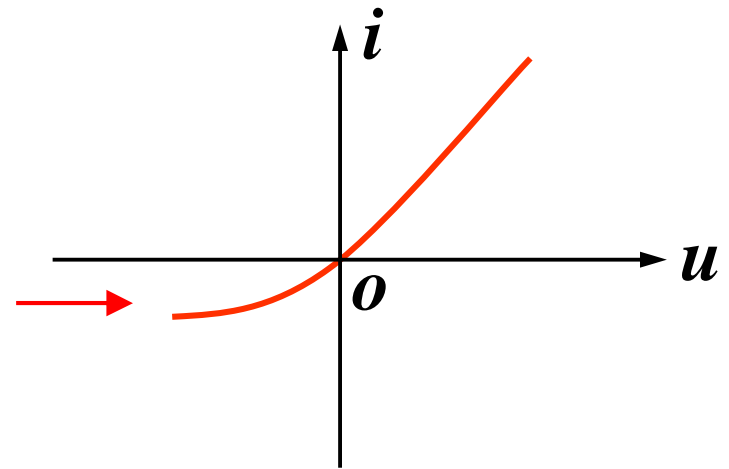

2.

• ()

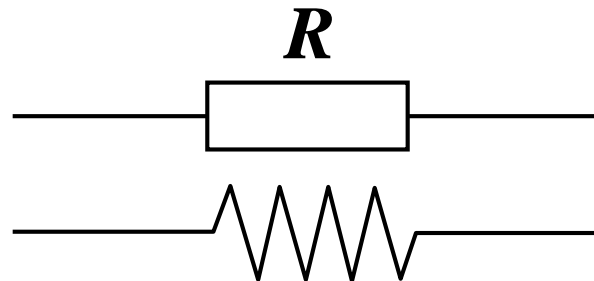

• $u \quad i$

$$R \quad \begin{matrix} u & i \\ i & \frac{u}{R} \end{matrix} \quad u \quad Ri$$

• R



$$u \quad V \quad i \quad A \quad R$$

$$G \quad \frac{1}{R}$$

$$i \quad Gu$$

G

$S(\quad)$

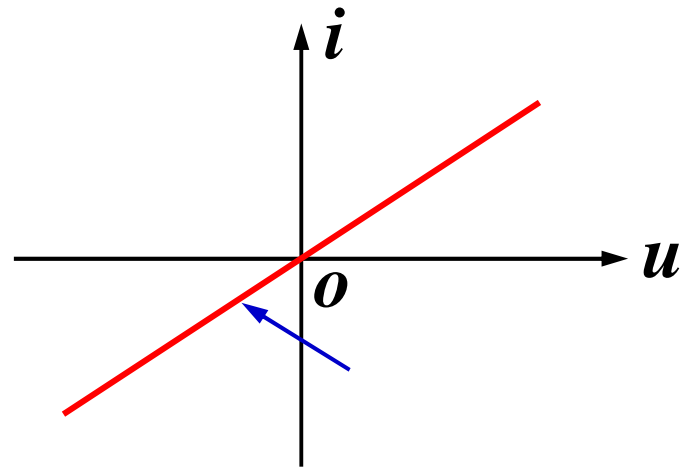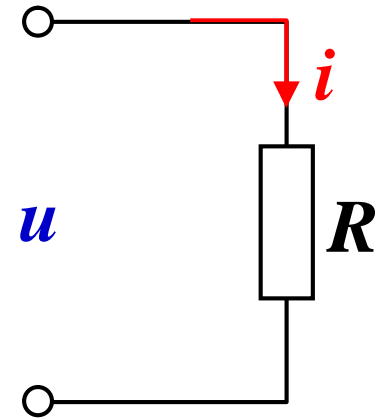


R G



(*R*)

u Ri or i Gu

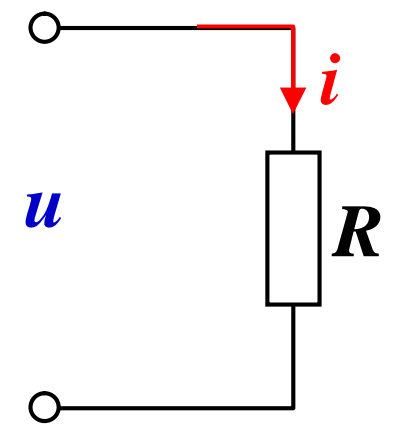

3.



•

u i

$$p \quad ui \quad Ri^2 \quad \frac{u^2}{R} \quad Gu^2 \quad \frac{i^2}{G}$$

u i
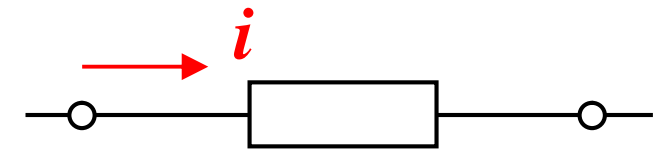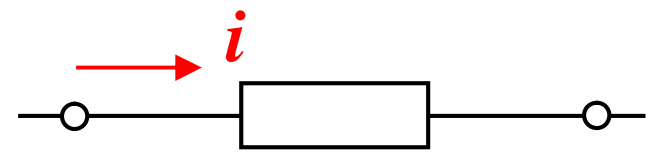
$$p \quad ui \quad Ri^2 \quad Ri^2 \quad \frac{u^2}{R}$$



•

t_0 t

$$w(t) = \int_{t_0}^t p \, dt = \int_{t_0}^t u(\cdot) i(\cdot) \, dt$$

4.

/

/

①

$$u = f(i)$$

$$i = f(u)$$



②

$$u(t) = R(t) i(t)$$

$$u = i$$


$$i(t) = G(t) u(t)$$

$$R(t)$$


③

5. ()

(1)

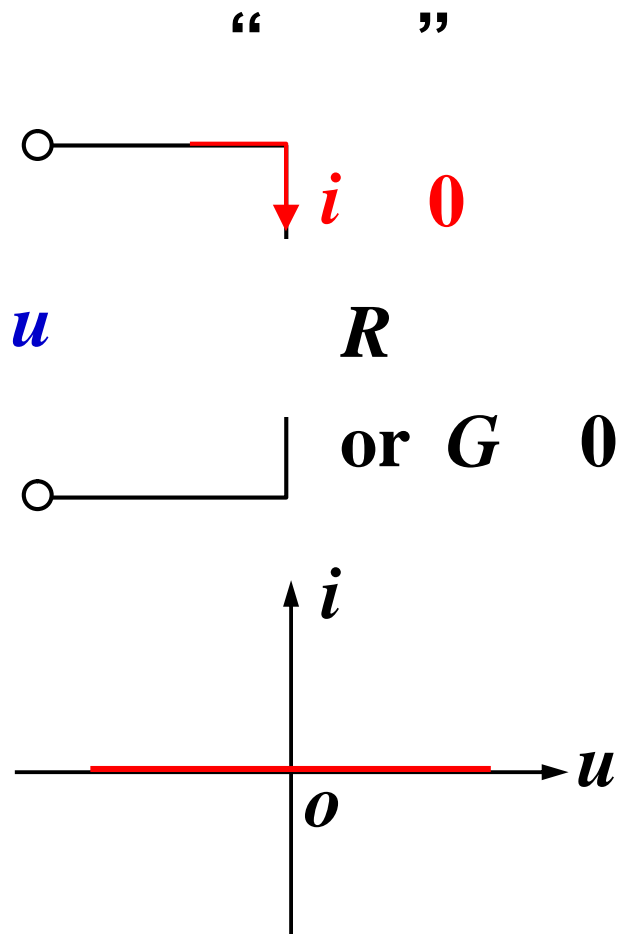

(2)

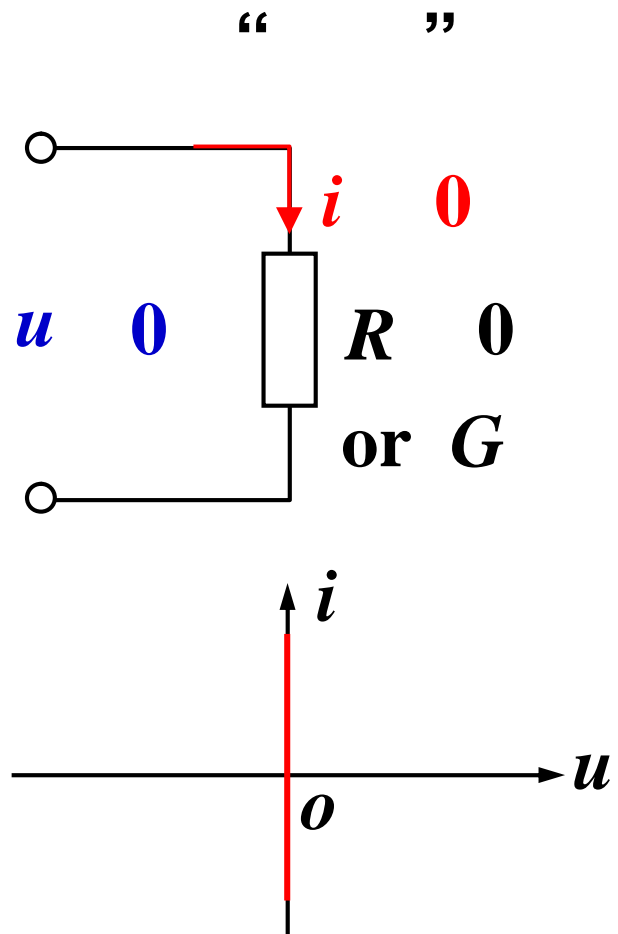












R *G*

u *R i* *i* *G u*

S

p *ui* *i²R* $\frac{u^2}{R}$

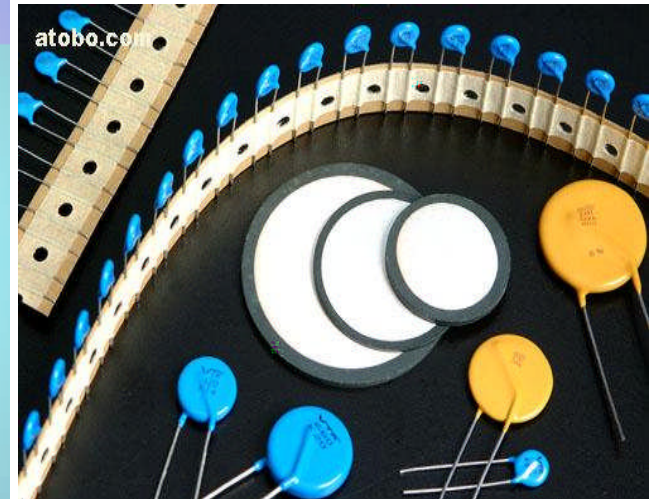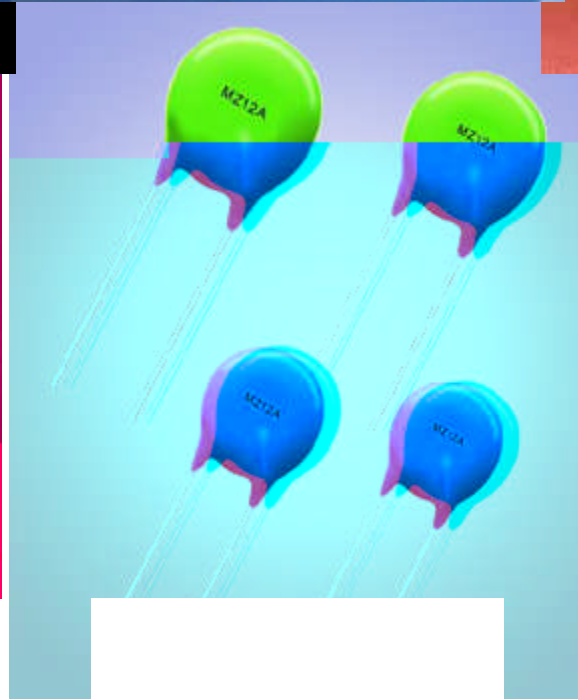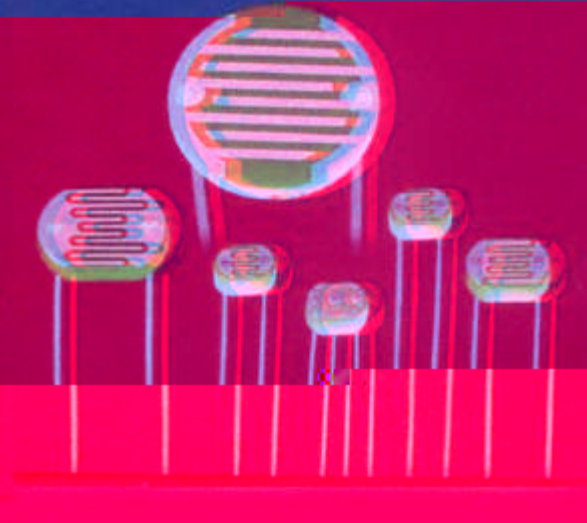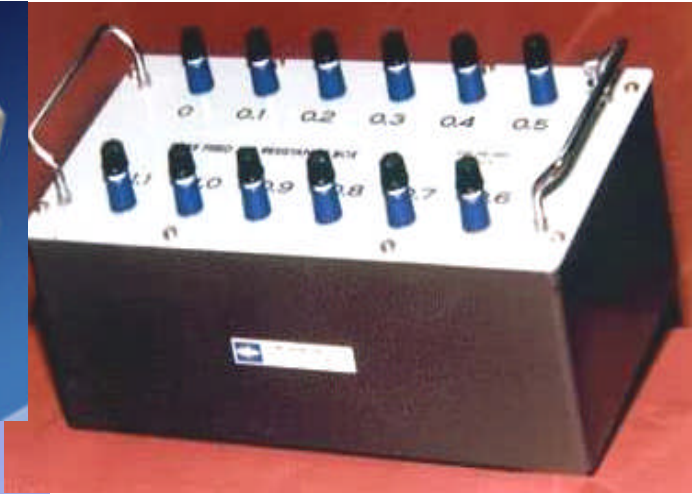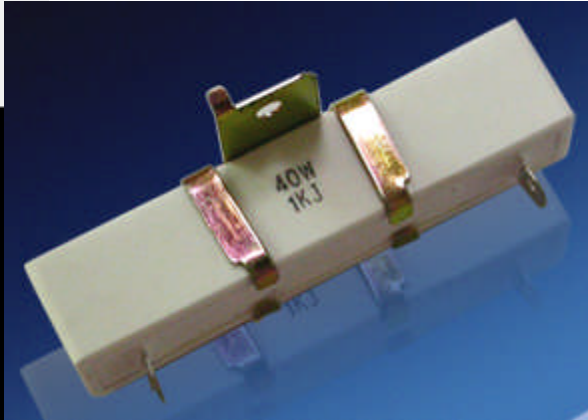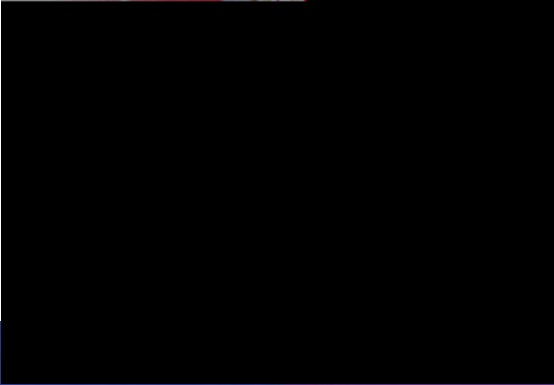


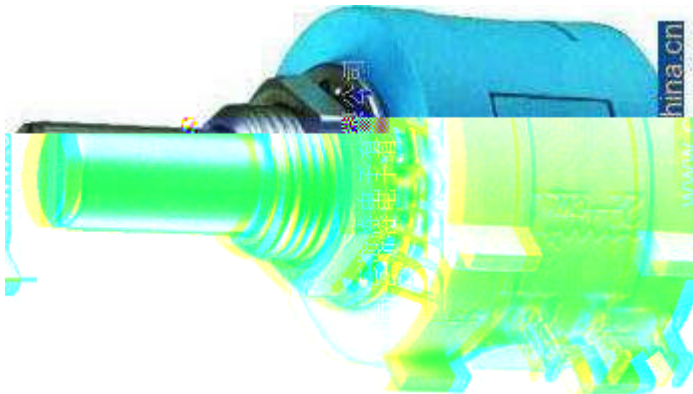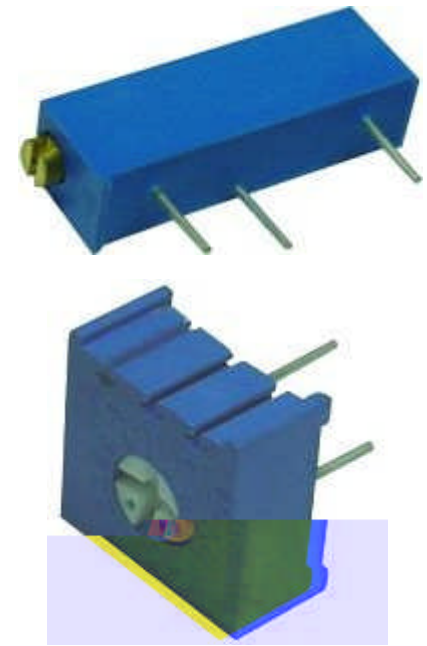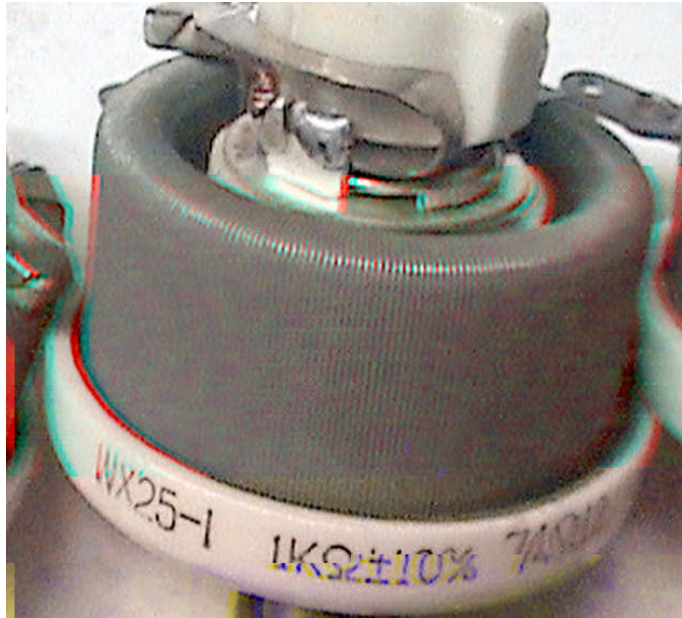



1 6

1.

i

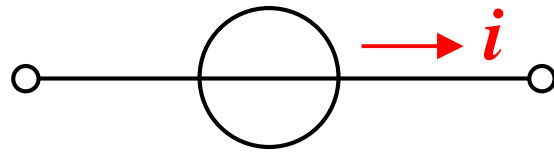


•

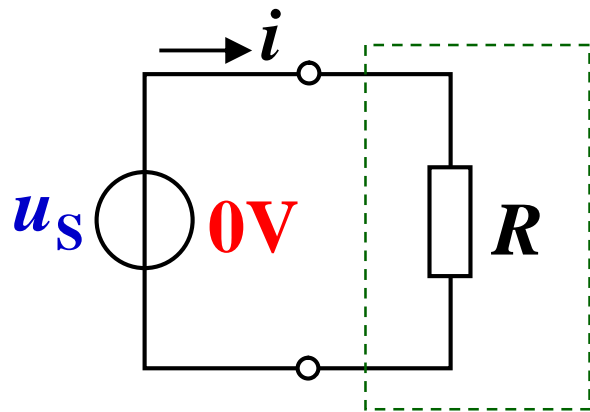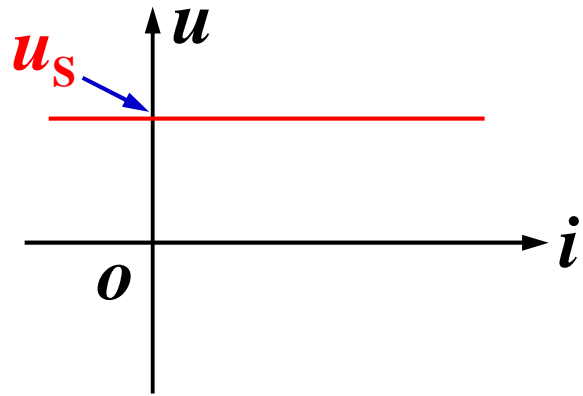

$$i = \frac{u_S}{R}$$

$$R = \left(\quad \right) i$$

$$R = \frac{u_S}{i}$$

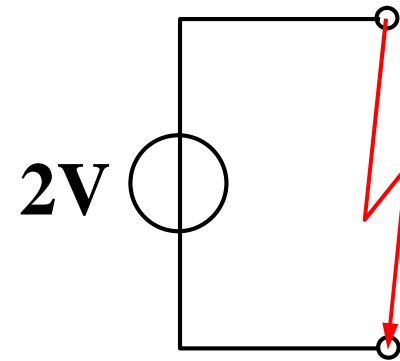

0 ?

2V ?

$u_S = 0$


$u_S = 0$

•


$$P = u_s i$$



()

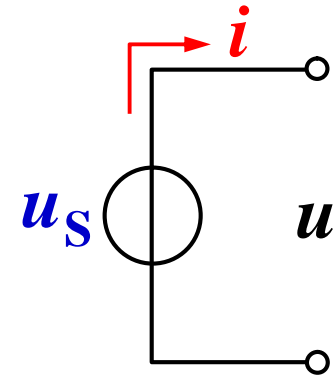

$$P = u_s i$$

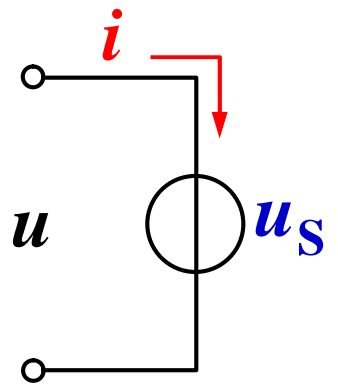

$$P = u_s i$$

$$u_R \quad \text{V}$$

$$i = \frac{u_R}{R} = \frac{5}{5} \quad \text{A}$$


$$P_{10V} = u_s i \quad \text{W}$$

$$P_{5V} = u_s i \quad \text{W}$$

$$P_R = Ri^2 \quad \text{W}$$

P


P

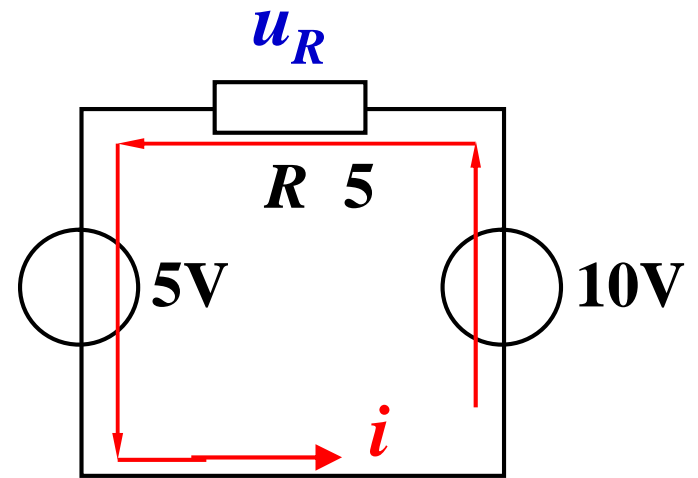

2.



•

u

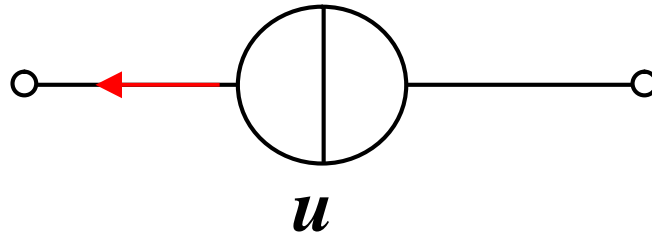

•


•

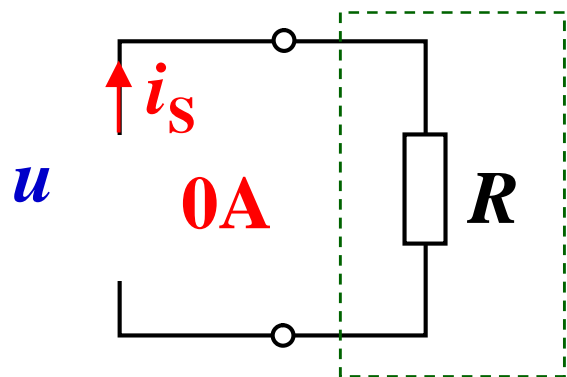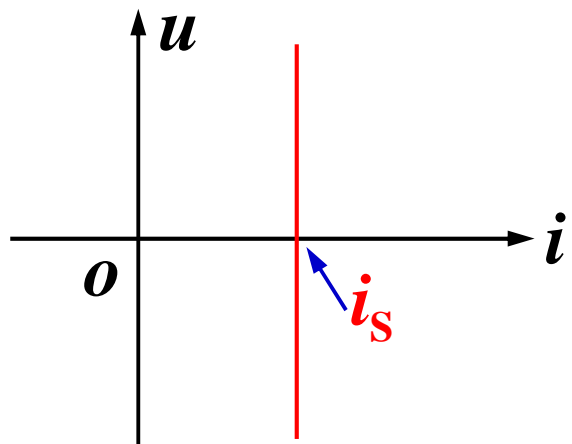

$$u \quad Ri_S$$

$$R \quad u \quad 0$$

$$R \quad u$$

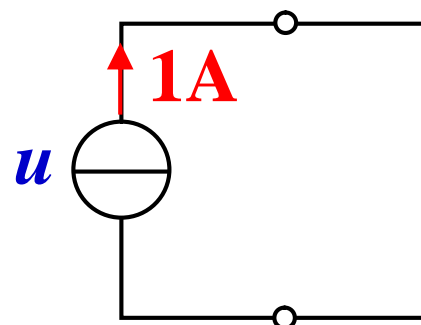


$$0 \quad ?$$


$$1A \quad ?$$

$$i_S \quad 0$$

$$i_S \quad 0$$

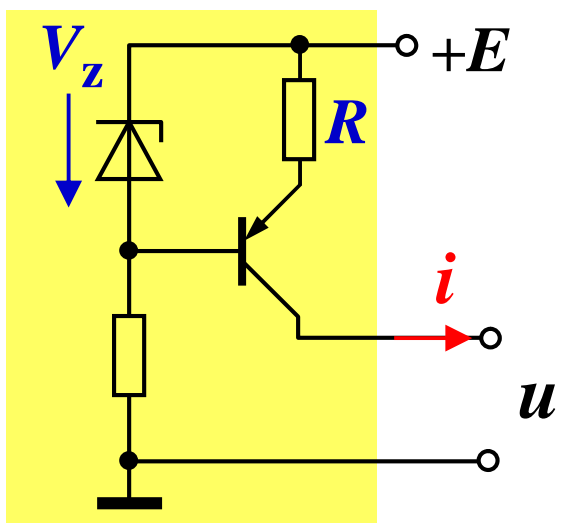

$$i \approx \frac{V_z}{R}$$


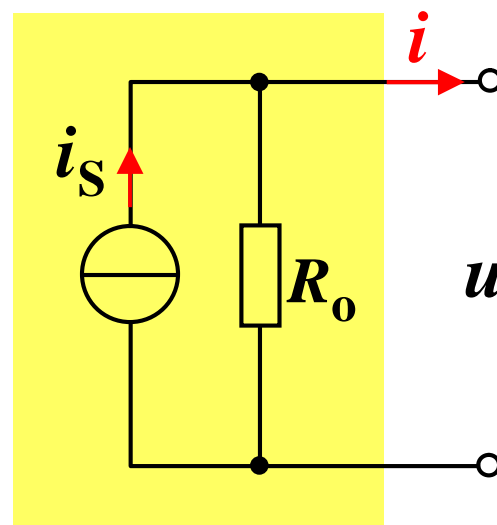



•

$$P = ui_s$$

$$P = ui_s$$

$$P = ui_s$$

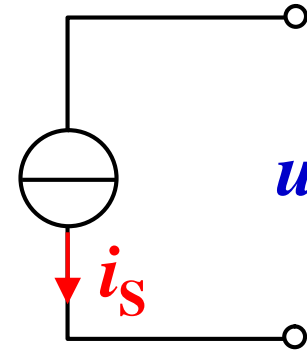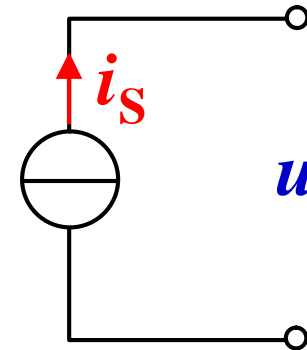

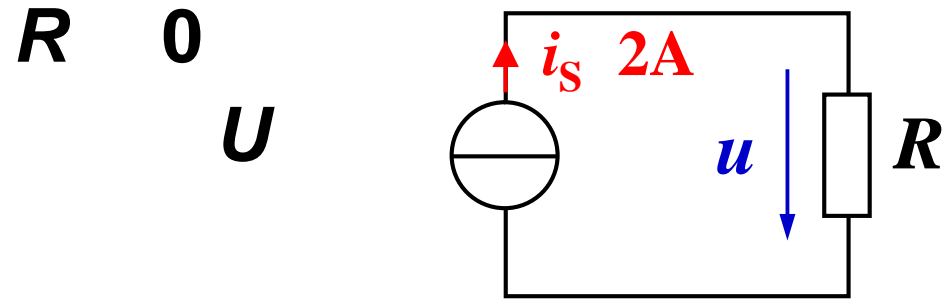

(1) $R \quad 0 \quad U$

$P \quad ui_s \quad i_s^2 R$




$R \quad u$

(2) $R \quad 0 \quad u \quad 0 \quad P \quad ui_s \quad 0$

(3) $R \quad u \quad P \quad ui_s$

i i_s
 u u_s $5V$

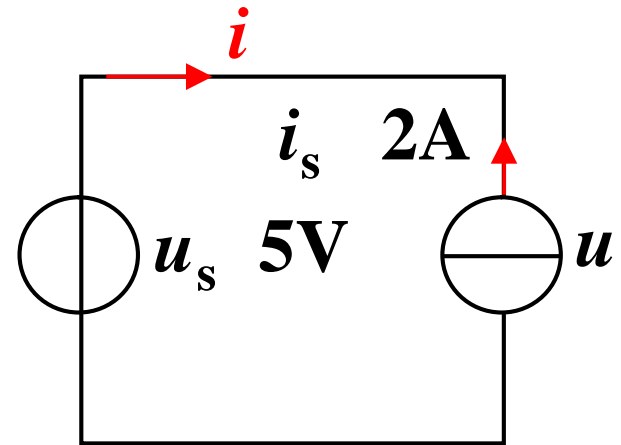

P_{2A} $u i_s$ W

P_{5V} $u_s i$ W

$5V$ $(10 W$
 $10W$


P P

3.

(1) ()




() **1.5V** ()

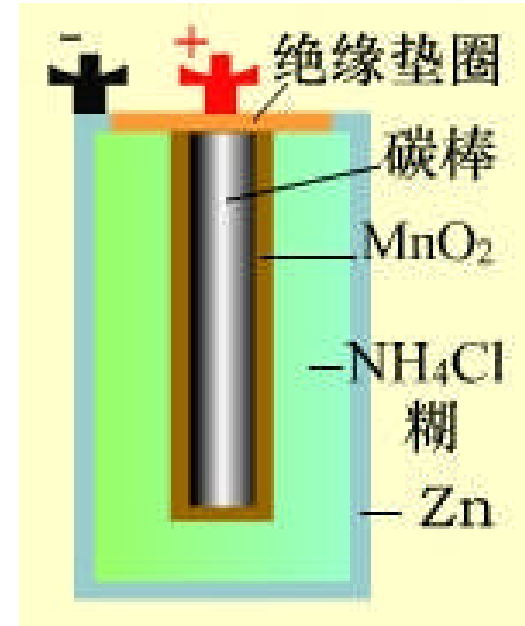


(2) ()




() **1.35V** ()

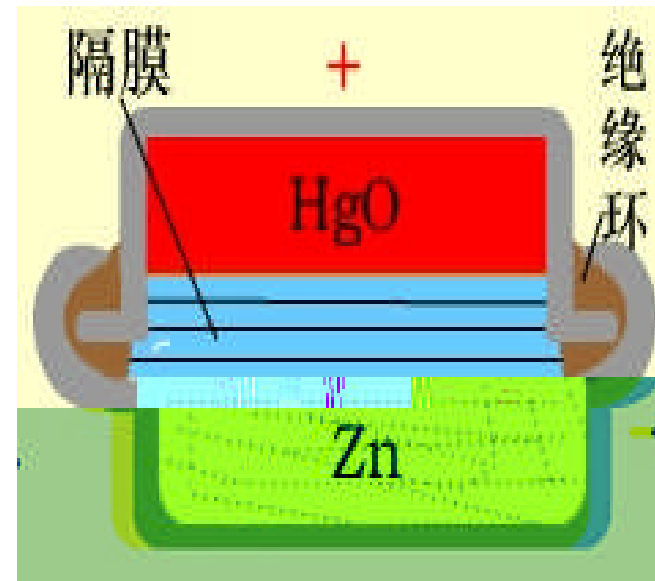

(3) ()
 1.23V
 40 45%

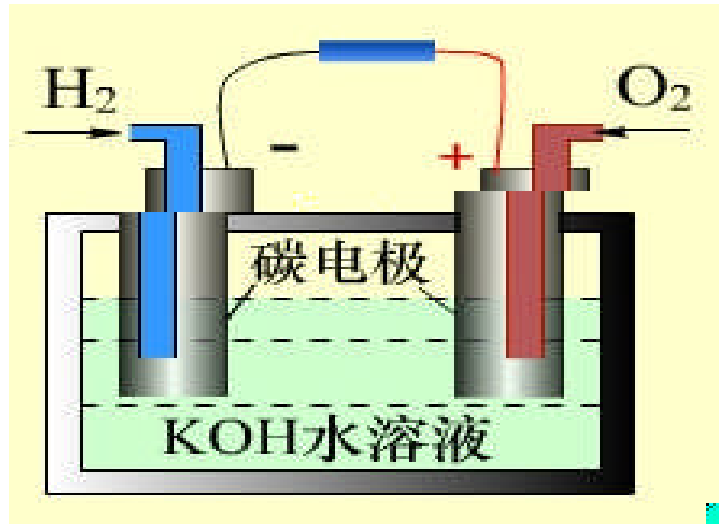

(4) ()
 P-N
 N P
 11%

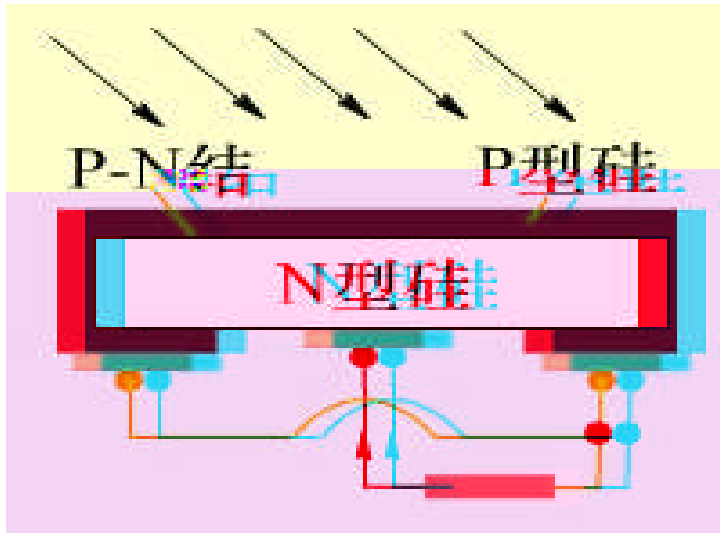



50cm²

0.6V

0.1A



F L D

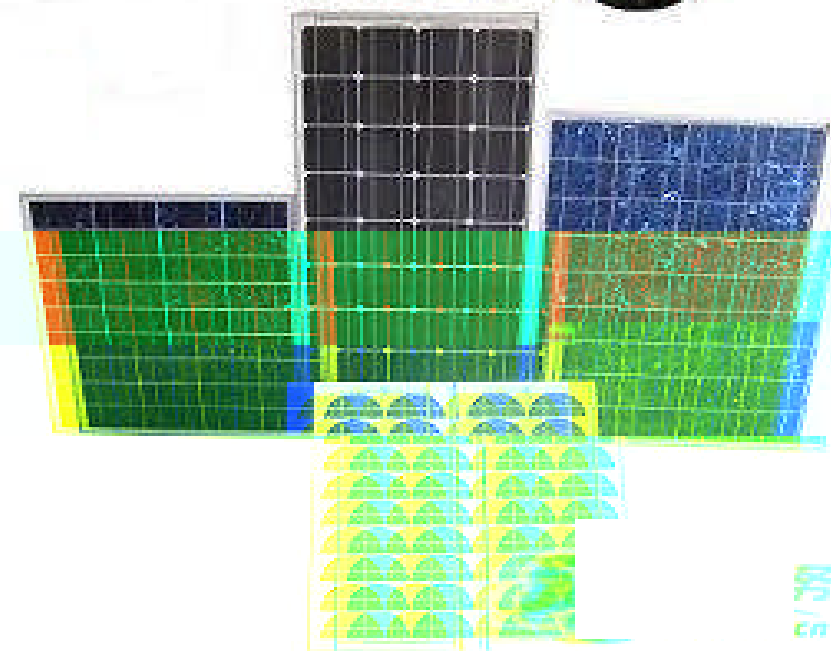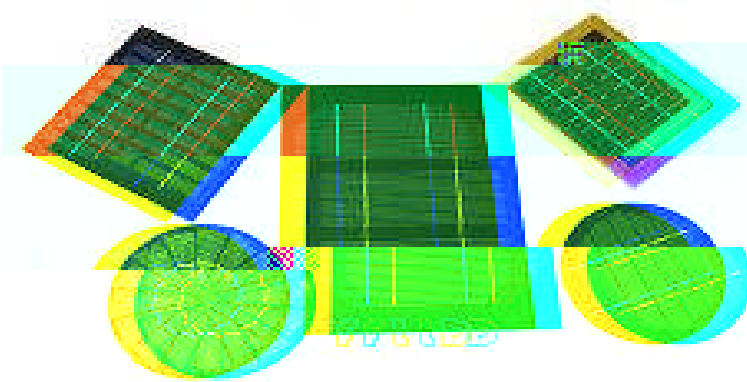


MC/5

(5) ()





2V

2V

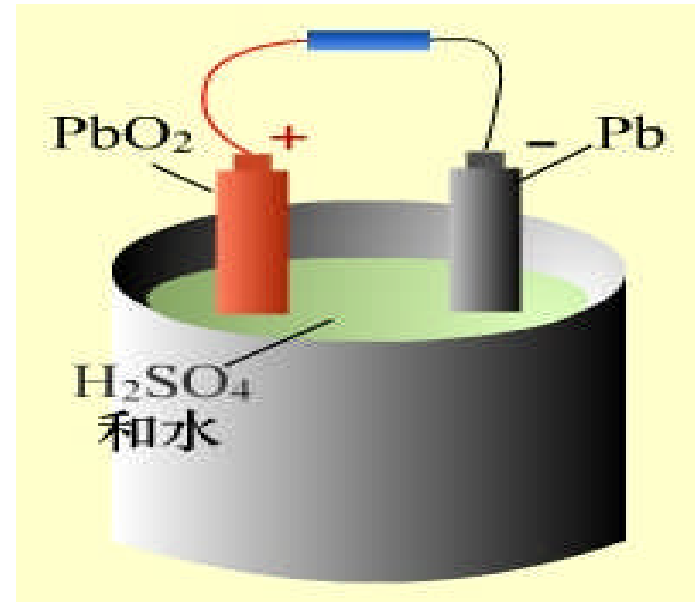

(6)

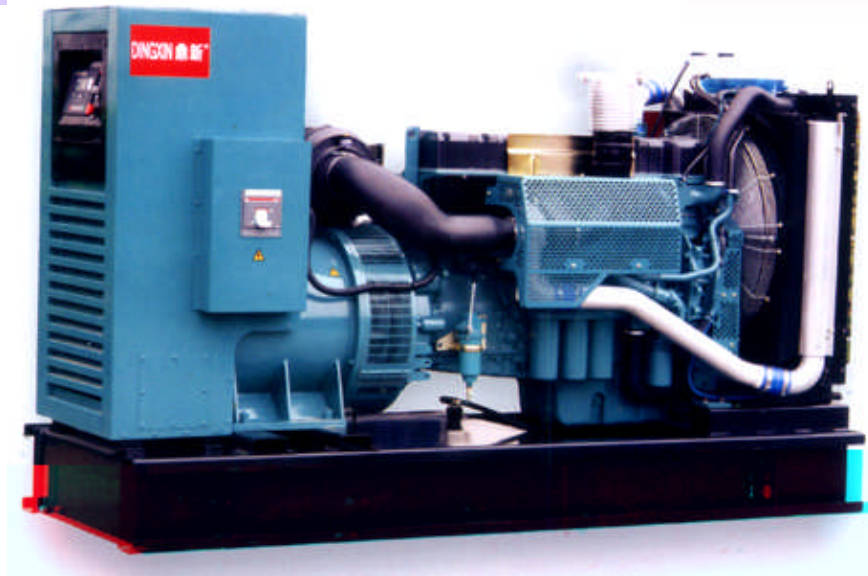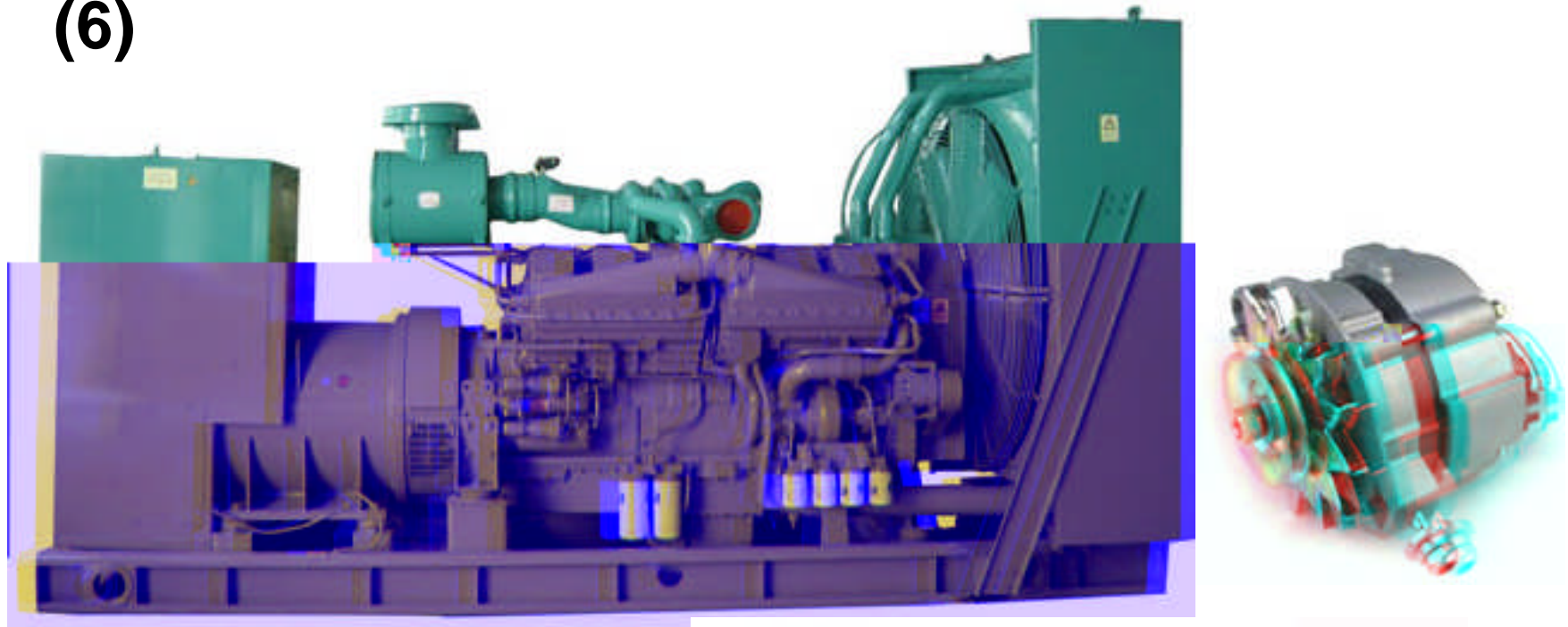



(7)





1 7 ()

1.

)

(

•

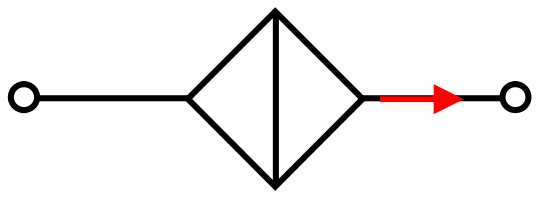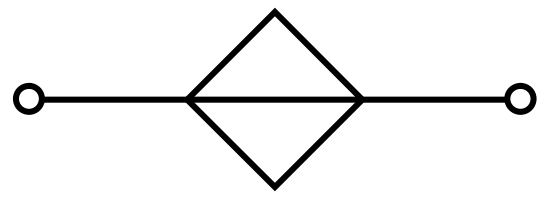

2.




u

i



(1)


(CCCS)

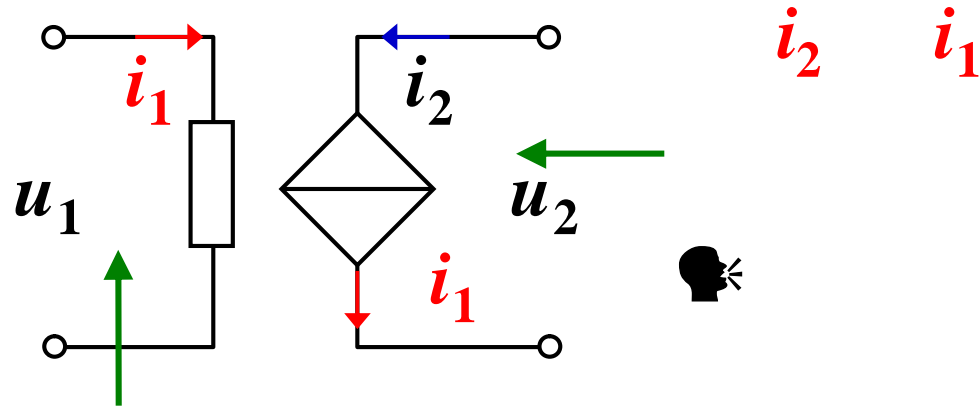

(i_c i_b)


(2)

(VCCS)

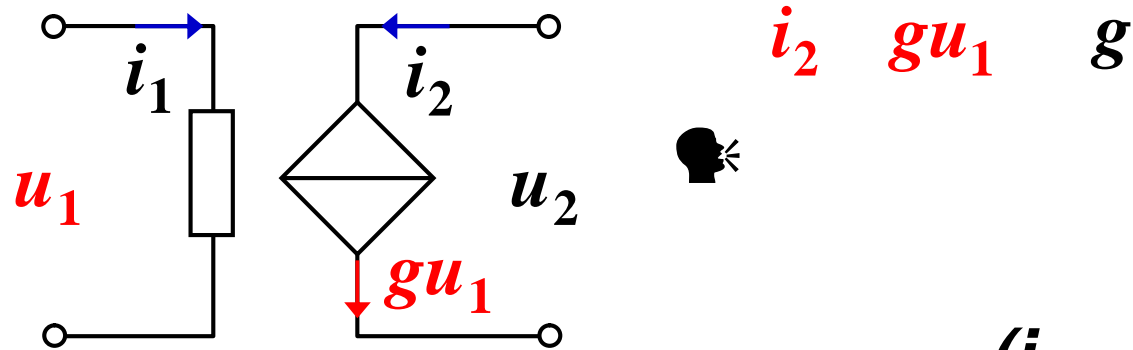

(i_d gu_{gs})

(3) (VCVS)

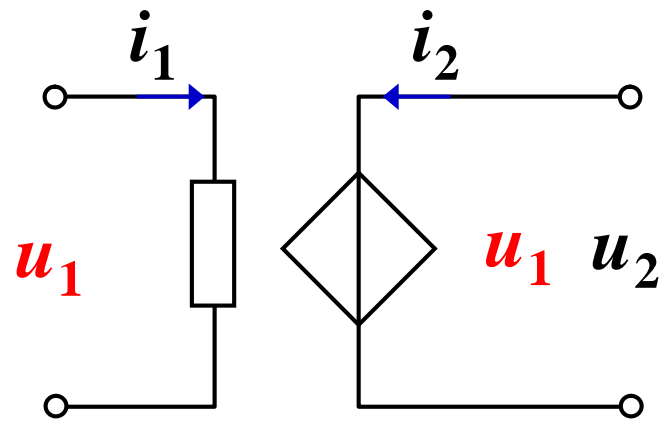


u_2 u_1

⦿

$(u_o \quad Au_d)$

(4) (CCVS)

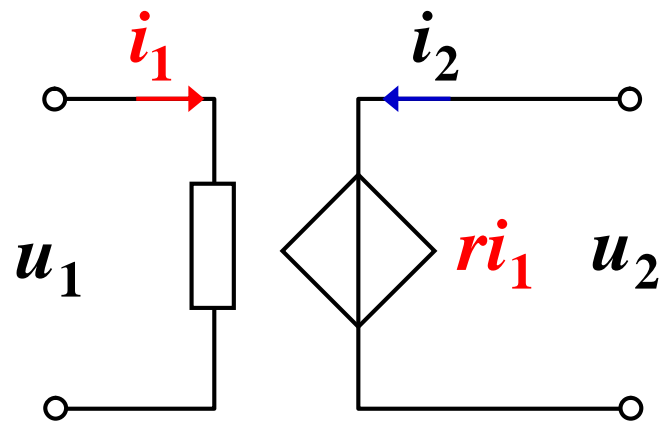

u_2 ri_1

r



⦿

$(u_o \quad ri_f)$



g r

“ ”

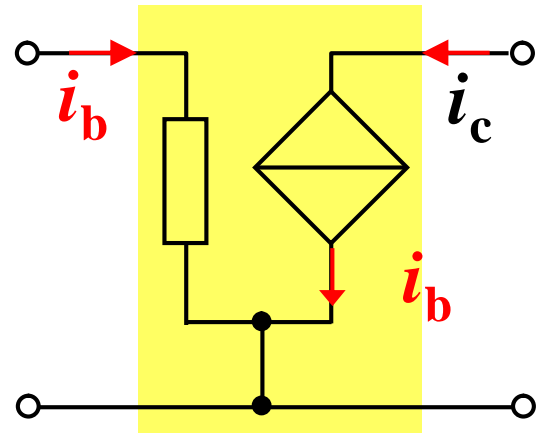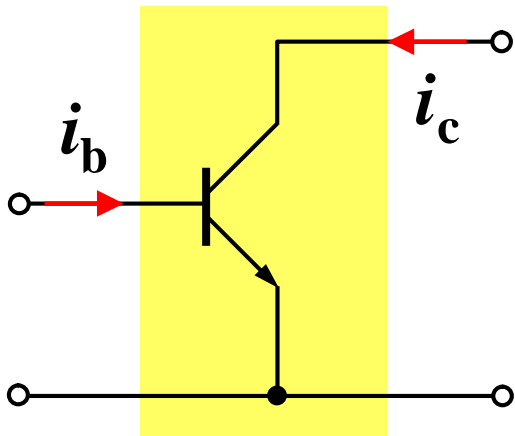

3.


()

(

)


“ ”

“ ”

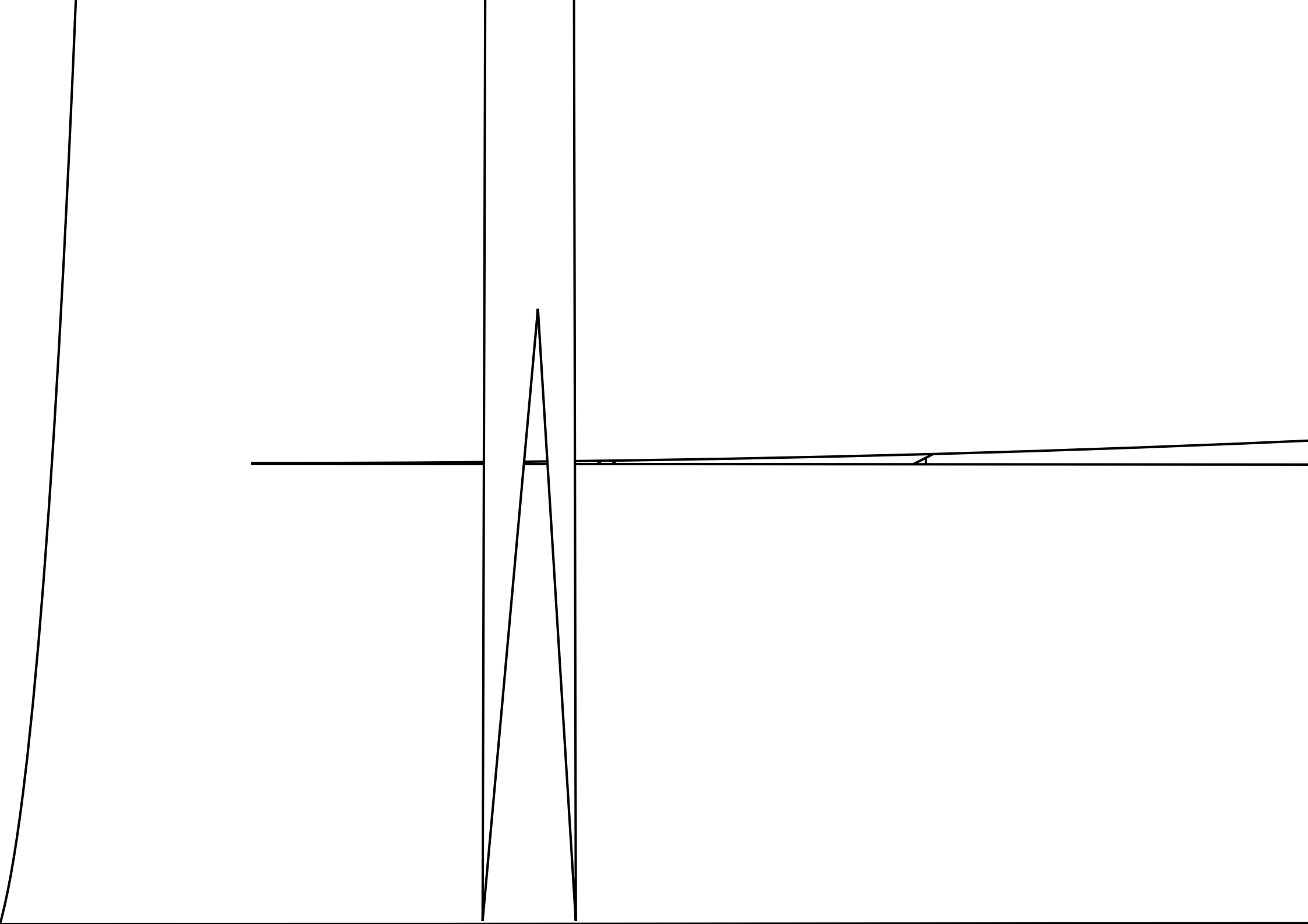

$$\begin{aligned}
 i_1 &= \frac{u_1}{3} + 2A \\
 u_2 &= 5i_1 + u_1 \\
 &\quad \times 2 \quad 6 \\
 &\quad \quad \quad V
 \end{aligned}$$

u_2 ?

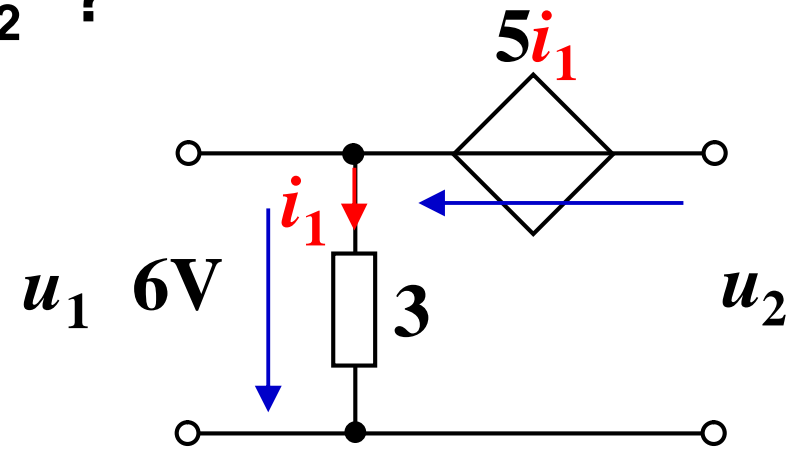

1-9

(KL)



(KVL)

(KCL)




(VCR)

u_R Ri_R

(KCL KVL)

KL VCR

1.
(1)

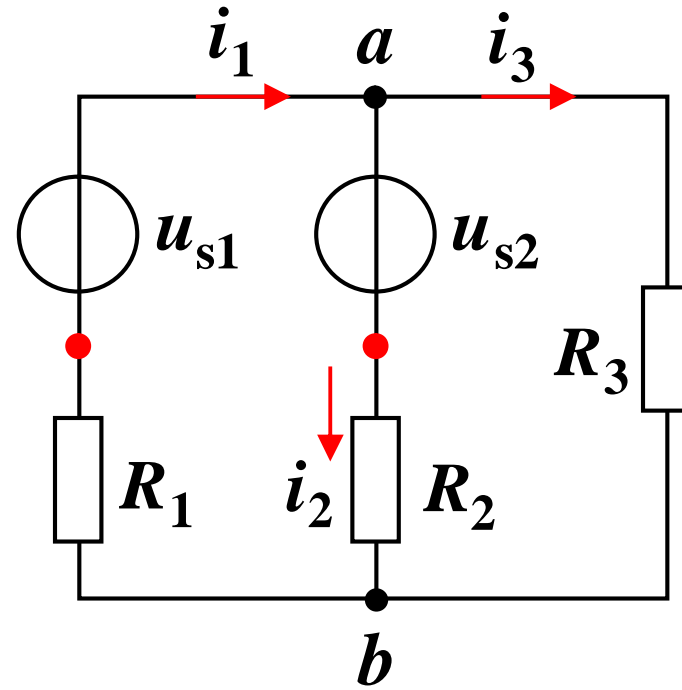

b 5

b 3

(2)

n 4

n 2




(3)

(4)


l_3

(5)

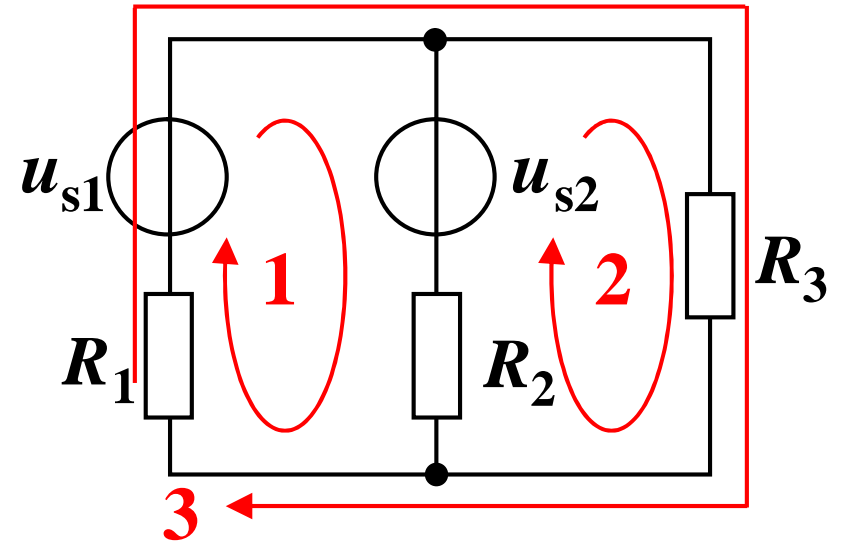

2. KCL ()

💡 **KL 1845**

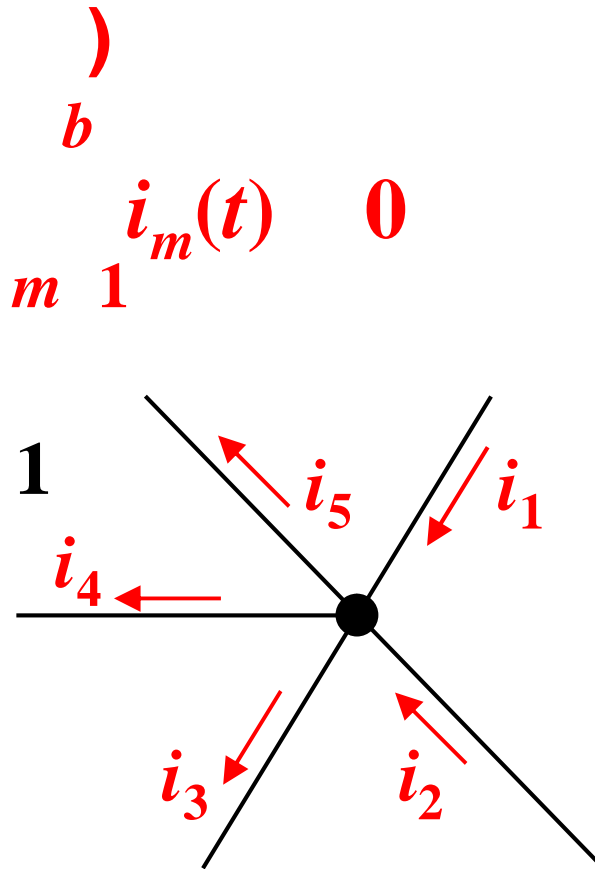

$$i_1 \quad i_2 \quad i_3 \quad i_4 \quad i_5 \quad 0$$

$$i_1 \quad i_2 \quad i_3 \quad i_4 \quad i_5$$

(

2

$$i_1 \quad i_2 \quad i_3 = 0$$

$$i_1 \quad \cancel{i_4} \quad \cancel{i_6} \quad 0$$

$$i_2 \quad \cancel{i_4} \quad \cancel{i_5} \quad 0$$


$$i_3 \quad \cancel{i_5} \quad \cancel{i_6} \quad 0$$

3

$$i_1 \quad i_2 \quad i_3 \quad 0$$



KCL

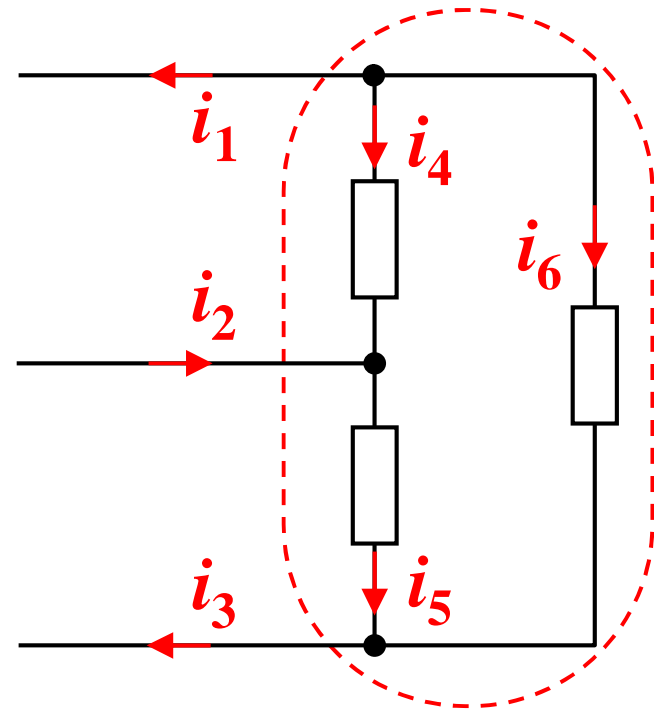




KCL

KCL

KCL



KCL

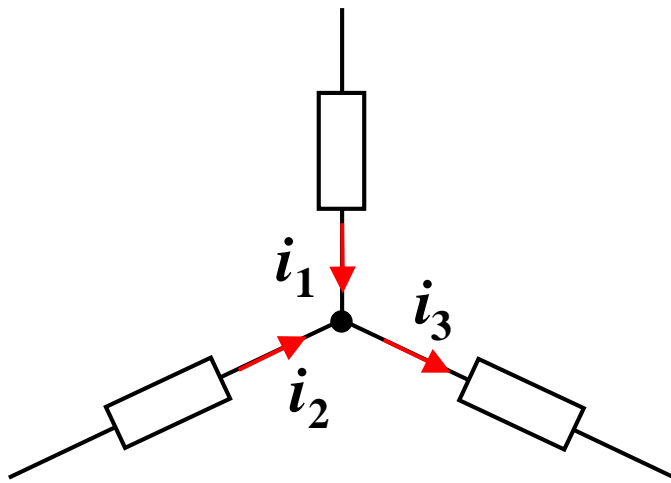

$$\begin{array}{cccc} i_2 & 2A & i_3 & 3A \\ i_1 & & & \\ i_1 & i_2 & i_3 & 0 \\ i_1 & i_2 & i_3 & \end{array}$$

2)

3.




(KVL)

$$\sum_{m=1}^n u_m(t) = 0$$

u u

(

)

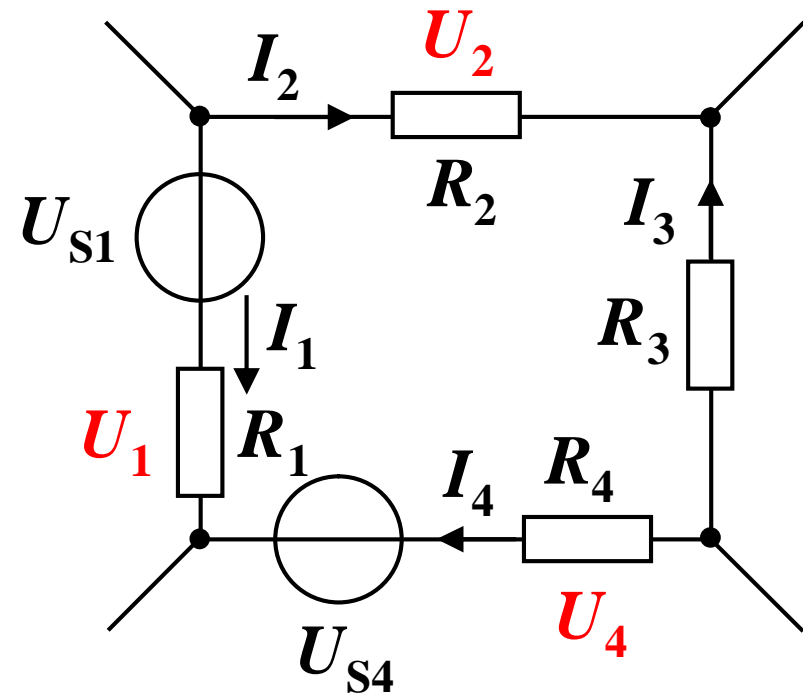

KVL


U_{13} U_S U_1 U_2



KVL

KVL

KVL

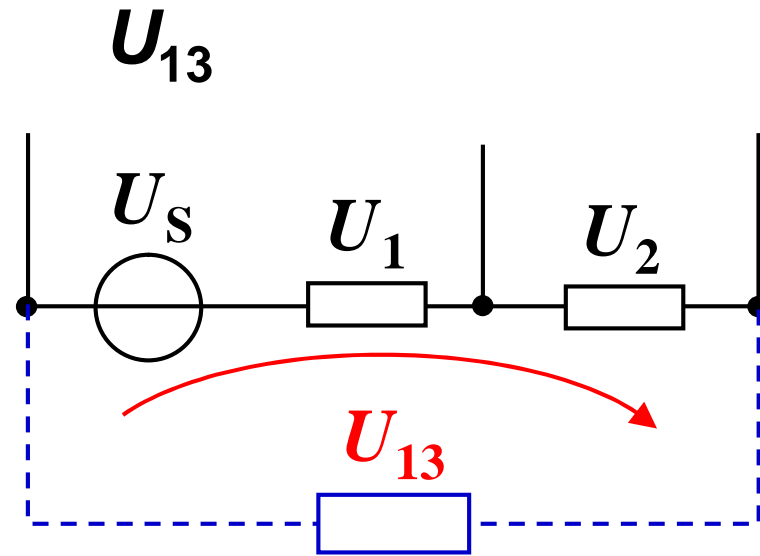

4. KCL KVL

KCL

KVL



KCL KVL

KCL

KVL

()

KCL KVL

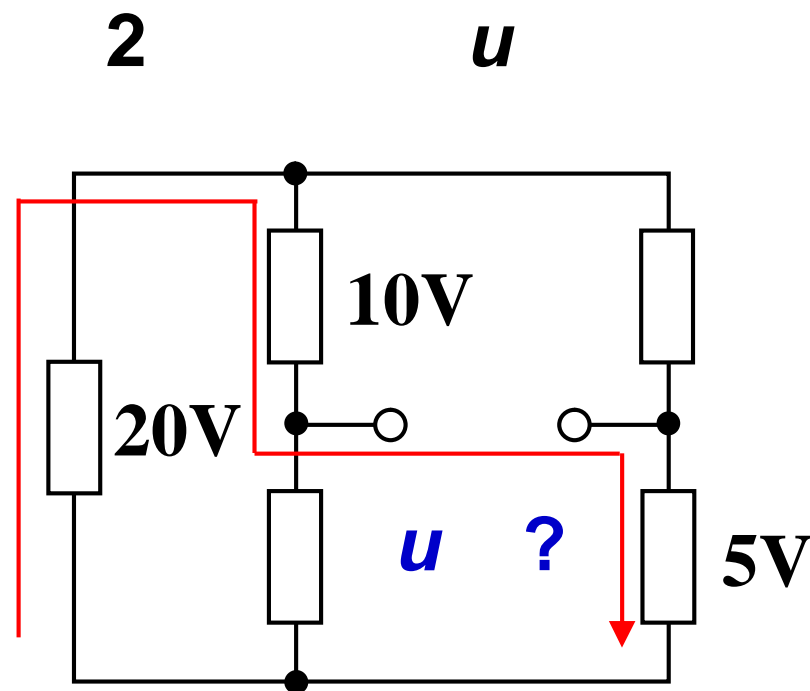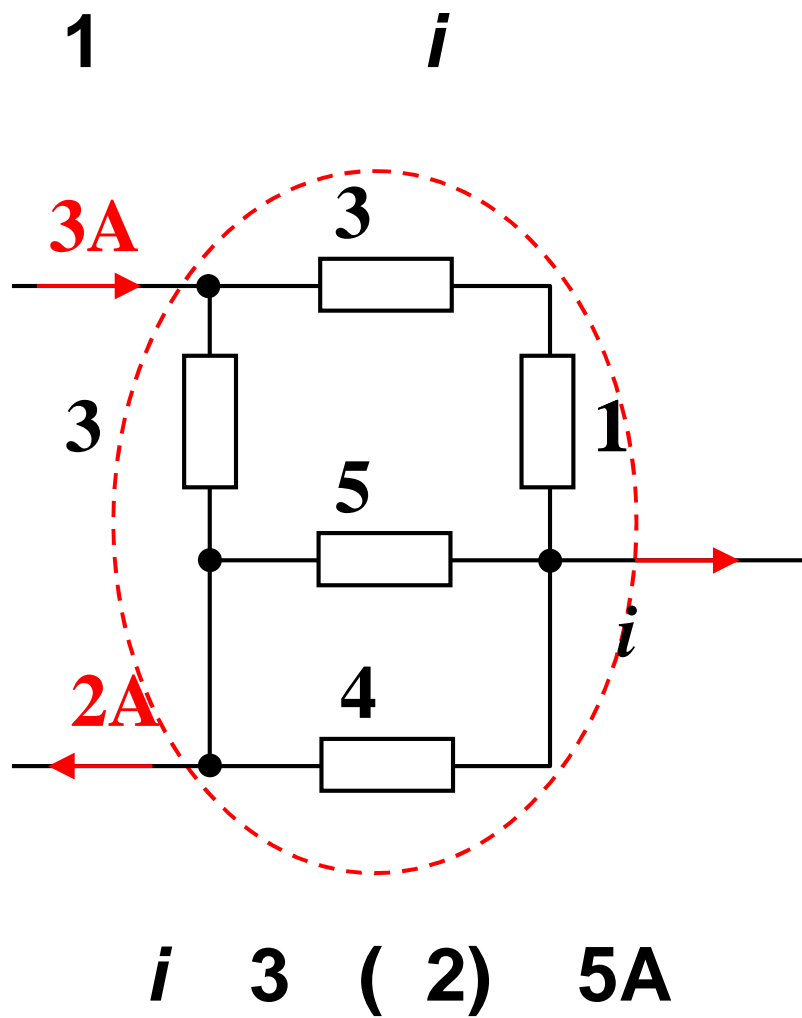


20	10	u	5	0
u	10	20	5	
	$15V$			

3

i

$3i$ 4 5


i 3A

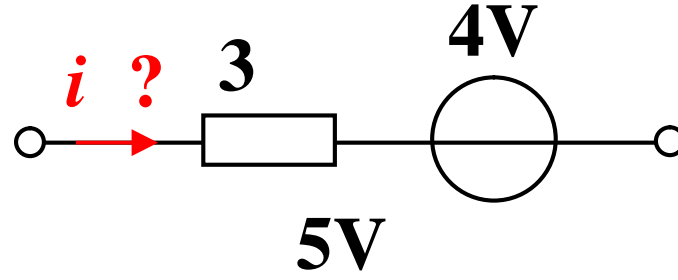


4

u


u 3 2 4

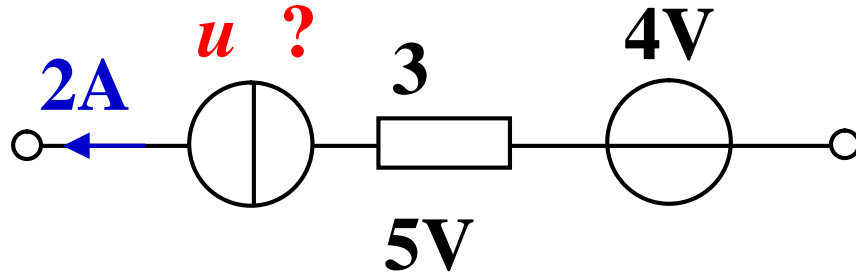

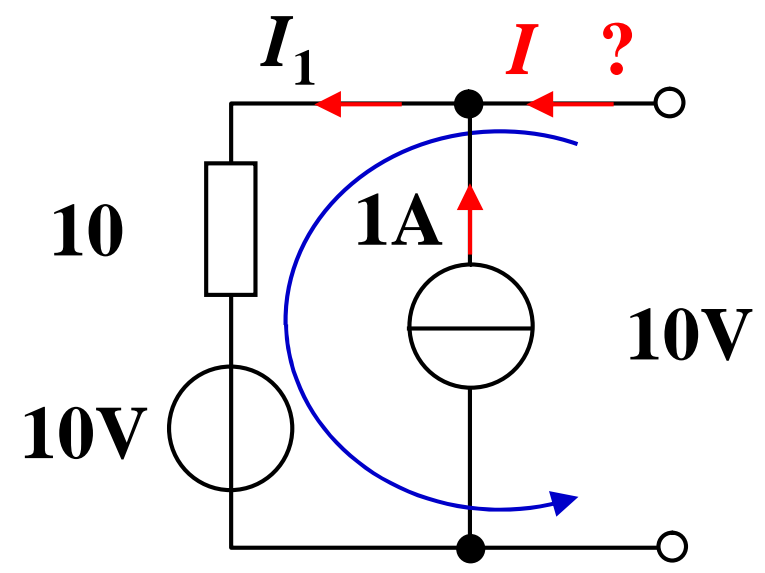
5 I
 $10I_1$ 10 10)
 I_1 2A
 I I_1 1 2 1 3A



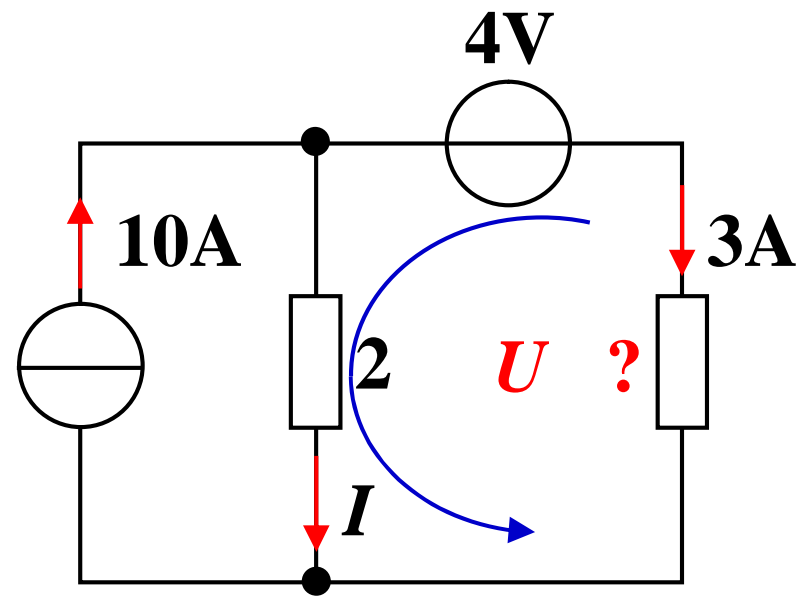6 U
 I 10 3 7A
 U 4 $2I$ 0
 U $2I$ 4
 14 4 10V



7

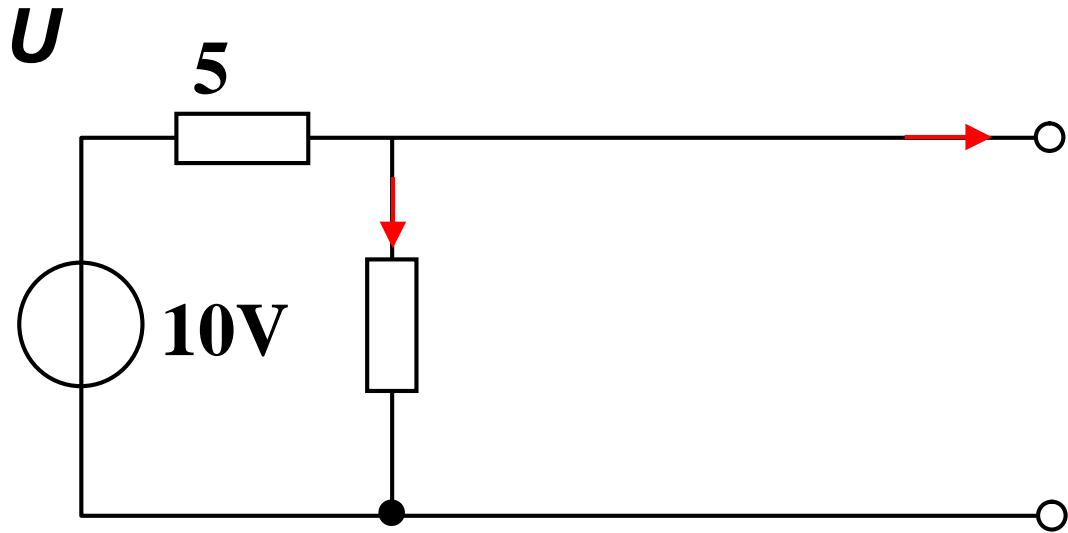

5


8

U

$$\begin{aligned}
 U & R_2 I_1 \\
 U_S & R_1(I_1 + I_1) \\
 I_1 & \frac{U_S}{R_1(1 + 1)}
 \end{aligned}$$

$$U = R_2 \frac{U_S}{R_1(1 + 1)}$$

$$\left| \frac{U}{U_S} \right| = \frac{R_2}{R_1} \frac{1}{2}$$

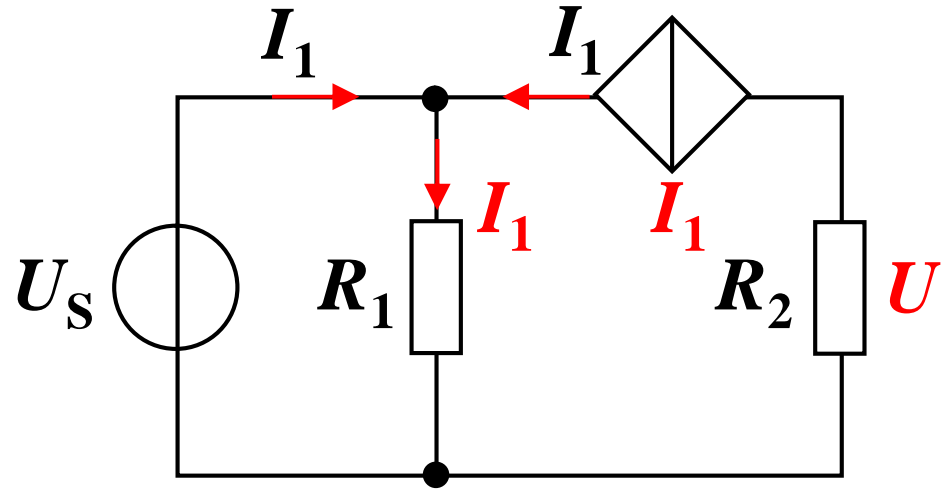

1.

2.

3.

p ui

4.

5.

(2)

(4)

6.

(VCR)

(KCL KVL)

